

R_1 R_2 R_3
a) $1\Omega, 2\Omega$ y 3Ω

EN SERIE $R = 1 + 2 + 3 = 6\Omega$

EN PARALELO:

$$\frac{1}{R} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R} = 1 + 0.5 + 0.33$$

$$\frac{1}{R} = 1.83$$

$$\frac{1}{1.83} = R$$

$$R = 0.55\Omega$$

$$\frac{1}{R} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3} = \frac{6}{6} + \frac{3}{6} + \frac{2}{6} = \frac{11}{6}$$

$$\frac{1}{1} = \frac{1 \cdot 6}{6} = \frac{6}{6}$$

$$\frac{1}{R} = \frac{11}{6}$$

$$\frac{1}{2} = \frac{1 \cdot 3}{2 \cdot 3} = \frac{3}{6}$$

$$1 = \frac{11 \cdot R}{6}$$

$$\frac{1}{3} = \frac{1 \cdot 2}{3 \cdot 2} = \frac{2}{6}$$

$$\frac{1 \cdot 6}{11} = R = \boxed{0.55 \Omega}$$


$$b) \frac{1}{R} = \frac{1}{4} + \frac{1}{6} + \frac{1}{8}$$

$$\frac{1}{R} = 0.25 + 0.1\hat{6} + 0.125$$

$$\frac{1}{R} = 0.541\hat{6}$$

$$\frac{1}{0.541\hat{6}} = R$$

$$R = 1.85 \Omega$$

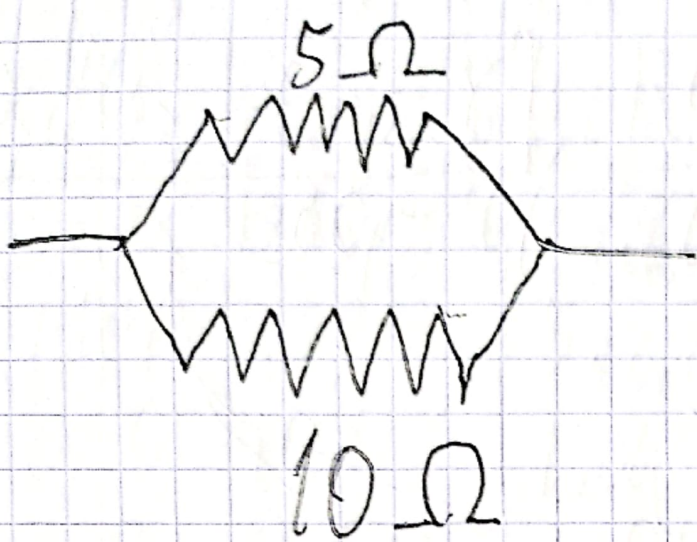

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\frac{1}{R} = \frac{1}{5} + \frac{1}{10}$$

$$\frac{1}{R} = 0.2 + 0.1 = 0.3$$

$$\frac{1}{R} = 0.3$$

$$\frac{1}{0.3} = R$$

$$R = 3.3\ \Omega$$

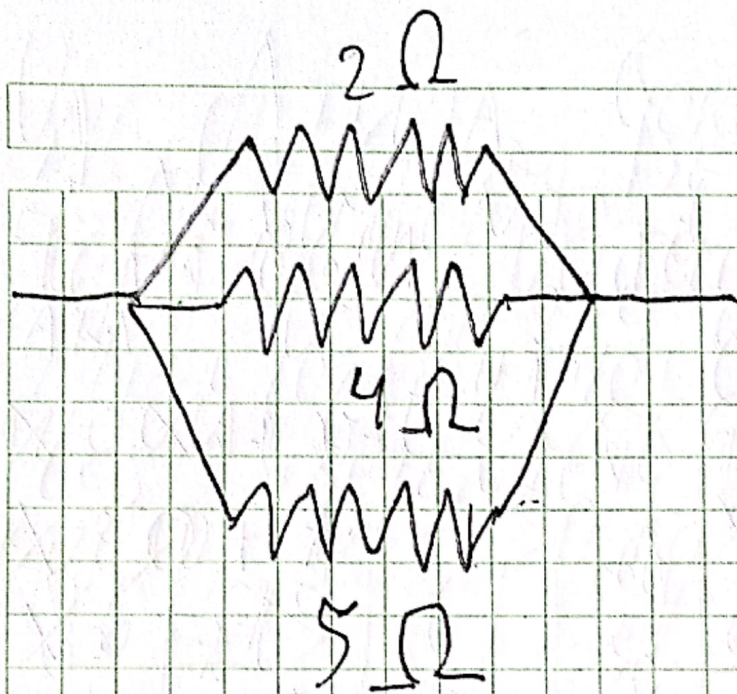

$$\frac{1}{R} = \frac{1}{2} + \frac{1}{4} + \frac{1}{5}$$

$$\frac{1}{R} = 0.5 + 0.25 + 0.2 = 0.95$$

$$R = \frac{1}{0.95} = 1.05 \Omega$$